## Cheat Sheet for EE464

## Performance Parameters

$$TruePowerFactor = \frac{P}{S} = DPF \frac{I_{1,RMS}}{I_{RMS}}$$
 
$$THD = \sqrt{(\frac{I_{rms}}{I_{1rms}})^2 - 1}$$

Symmetry	Condition Required	$a_h$ and $b_h$
Even	f(-t) = f(t)	$b_h = 0$ $a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$
Odd	f(-t) = -f(t)	$a_h = 0$ $b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0 \text{ for even } h$ $a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t) \text{ for odd } h$ $b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t) \text{ for odd } h$

Figure 1: Fourier Transform Table

## Switch Selection

**Peak Switch Current** 

$$\hat{I}_{sw} = rac{1}{(1-D)} rac{N_2}{N_1} I_o + rac{N_1}{N_2} rac{(1-D)T_s}{2L_m} V_o$$

Peak Switch Voltage

$$\hat{V}_{sw} = V_d + rac{N_1}{N_2} V_o = rac{V_d}{(1-D)}$$

Figure 2: Flyback switch considerations

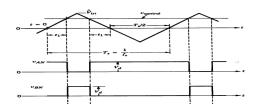


Figure 3: Bipolar Switching

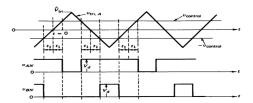


Figure 4: Unipolar switching

$$SwitchUtilization = \frac{Po}{Psw} = \frac{Io.Vo}{q.Vswmax.Iswmax}$$
 (1)

$$\begin{split} V_o &= V_s \bigg(\frac{D}{1-D}\bigg) \bigg(\frac{N_2}{N_1}\bigg) \\ &= \frac{D}{RCf} \\ I_{L_{m,\max}} &= I_{L_m} + \frac{\Delta i_{L_m}}{2} \\ &= \frac{V_s D}{(1-D)^2 R} \bigg(\frac{N_2}{N_1}\bigg)^2 + \frac{V_s DT}{2L_m} \\ I_{L_{m,\min}} &= I_{L_m} - \frac{\Delta i_{L_m}}{2} \quad \text{equate this to zero for dom boundary} \\ &= \frac{V_s D}{(1-D)^2 R} \bigg(\frac{N_2}{N_1}\bigg)^2 - \frac{V_s DT}{2L_m} \\ \Delta V_{O, \text{ESR}} &= \Delta i_C r_C = I_{L_{m,\max}} \bigg(\frac{N_1}{N_2}\bigg) r_C \end{split}$$

Figure 5: Flyback Formulas

$$\begin{bmatrix} V_o = V_s D \left( \frac{N_2}{N_1} \right) \end{bmatrix} \begin{bmatrix} \frac{\Delta V_o}{V_o} = \frac{1 - D}{8L_x C f^2} \end{bmatrix}$$

$$\Delta V_{o, ESR} = \Delta i_C r_C = \Delta i_{L_x} r_C = \left[ \frac{V_o (1 - D)}{L_x f} \right] r_C$$

$$\Delta i_{L_m} = \frac{V_s DT}{L_m}$$

Figure 6: Forward (single switched) Converter Formulas

$$\begin{bmatrix} V_o = 2V_s \left(\frac{N_S}{N_P}\right) D \end{bmatrix} \begin{bmatrix} \frac{\Delta V_o}{V_o} = \frac{1 - 2D}{32L_x C f^2} \end{bmatrix}$$

$$\Delta V_{o,ESR} = \Delta i_{L_x} r_C = \begin{bmatrix} \frac{V_o \left(\frac{1}{2} - D\right)}{L_x f} \end{bmatrix} r_C$$

Figure 7: Push Pull Formulas