

Cheat Sheet for EE464

$$\begin{aligned} \text{FormFactor} &= \frac{V_{rms}}{V_{avg}} \\ \text{CrestFactor} &= \frac{V_{peak}}{V_{rms}} \\ \text{DistortionFactor} &= \frac{I_{1rms}}{I_{rms}} \end{aligned}$$

ϕ : phase difference between fundamentals of current and voltage

$$\text{DisplacementPowerFactor} = \cos(\phi)$$

$$\text{TruePowerFactor} = \frac{P}{S} = \text{DPF} \frac{I_{1,RMS}}{I_{RMS}}$$

$$\text{THD} = \sqrt{\left(\frac{I_{rms}}{I_{1rms}}\right)^2 - 1}$$

Converters

$$\begin{aligned} V_o &= V_s \left(\frac{D}{1-D} \right) \left(\frac{N_2}{N_1} \right) & \frac{\Delta V_o}{V_o} &= \frac{D}{RCf} & (L_m)_{\min} &= \frac{(1-D)^2 R}{2f} \left(\frac{N_1}{N_2} \right)^2 \\ I_{L_m, \max} &= I_{L_m} + \frac{\Delta i_{L_m}}{2} & L_m &= \frac{V_s DT}{\Delta i_{L_m}} = \frac{V_s D}{\Delta i_{L_m} f} \\ &= \frac{V_s D}{(1-D)^2 R} \left(\frac{N_2}{N_1} \right)^2 + \frac{V_s DT}{2L_m} & \left(\Delta i_{L_m} \right)_{\text{desired}} &= \frac{V_s D}{L_m} \\ I_{L_m, \min} &= I_{L_m} - \frac{\Delta i_{L_m}}{2} & \text{equate this to zero for dcm boundary} & & \left(\Delta i_{L_m} \right)_{\text{desired}} &= \frac{V_s D}{L_m} \\ &= \frac{V_s D}{(1-D)^2 R} \left(\frac{N_2}{N_1} \right)^2 - \frac{V_s DT}{2L_m} & & & & \\ \Delta V_{o, \text{ESR}} &= \Delta i_C r_C = I_{L_m, \max} \left(\frac{N_1}{N_2} \right) r_C & & & & \end{aligned}$$

Figure 1: Flyback Formulas

$$\begin{aligned} V_o &= V_s D \left(\frac{N_2}{N_1} \right) & \frac{\Delta V_o}{V_o} &= \frac{1-D}{8L_x C f^2} \end{aligned}$$

$$\begin{aligned} \Delta V_{o, \text{ESR}} &= \Delta i_C r_C = \Delta i_{L_x} r_C = \left[\frac{V_o (1-D)}{L_x f} \right] r_C \\ \Delta i_{L_m} &= \frac{V_s DT}{L_m} \end{aligned}$$

Figure 2: Forward (single switched) Converter Formulas

$$\begin{aligned} V_o &= 2V_s \left(\frac{N_S}{N_P} \right) D & \frac{\Delta V_o}{V_o} &= \frac{1-2D}{32L_x C f^2} \\ \Delta V_{o, \text{ESR}} &= \Delta i_{L_x} r_C = \left[\frac{V_o \left(\frac{1}{2} - D \right)}{L_x f} \right] r_C \end{aligned}$$

Figure 3: Push Pull Formulas

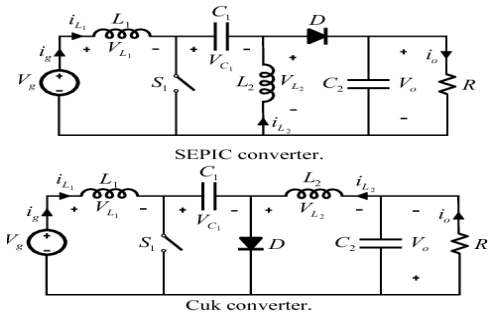


Figure 4: Sepic and Cuk Converter Schematics

$$\text{SwitchUtilization} = \frac{P_o}{P_{sw}} = \frac{I_o V_o}{q V_{swmax} I_{swmax}} \quad (1)$$

Inverters

$$m_f = \frac{f_s}{f_1}, m_a = \frac{V_{control}}{V_{triangle}}$$

$$\begin{aligned} V_o &= V_s \left(\frac{D}{1-D} \right) & \Delta V_{C1} &= \frac{I_o DT}{C} = \frac{V_o D}{RC_1 f} \\ \Delta i_{L1} &= \frac{V_s DT}{L_1} = \frac{V_s D}{L_1 f} & \Delta V_o &= \Delta V_{C2} = \frac{V_o D}{RC_2 f} \\ \Delta i_{L2} &= \frac{V_s DT}{L_2} = \frac{V_s D}{L_2 f} & C_1 &= \frac{D}{R(\Delta V_{C1}/V_o) f} \\ & & C_2 &= \frac{D}{R(\Delta V_o/V_o) f} \end{aligned}$$

Figure 5: Sepic Converter Formulas

$$\begin{aligned} V_o &= -V_s \left(\frac{D}{1-D} \right) & \frac{\Delta V_o}{V_o} &= \frac{1-D}{8L_2 C_2 f^2} \\ \Delta v_{C1} &\approx \frac{1}{C_1} \int_{DT}^T I_{L1} d(t) = \frac{I_{L1}}{C_1} (1-D) T = \frac{V_s}{RC_1 f} \left(\frac{D^2}{1-D} \right) \\ & & \Delta v_{C1} &\approx \frac{V_o D}{RC_1 f} \\ \Delta i_{L1} &= \frac{V_s DT}{L_1} = \frac{V_s D}{L_1 f} & \Delta i_{L2} &= \frac{V_s DT}{L_2} = \frac{V_s D}{L_2 f} \\ L_{1, \min} &= \frac{(1-D)^2 R}{2Df} & L_{2, \min} &= \frac{(1-D)R}{2f} \end{aligned}$$

Figure 6: Cuk Converter Formulas

Switch Selection

Peak Switch Current

$$\hat{I}_{sw} = \frac{1}{(1-D)} \frac{N_2}{N_1} I_o + \frac{N_1}{N_2} \frac{(1-D)T_s}{2L_m} V_o$$

Peak Switch Voltage

$$\hat{V}_{sw} = V_d + \frac{N_1}{N_2} V_o = \frac{V_d}{(1-D)}$$

Figure 7: Flyback switch considerations

$$\begin{aligned} V_o &= 2V_s \left(\frac{N_S}{N_P} \right) D & V_o &= V_s \left(\frac{N_S}{N_P} \right) D \\ \text{Full Bridge} & & \text{Half Bridge} & \end{aligned}$$

Figure 8: Full and Half Bridge Relations

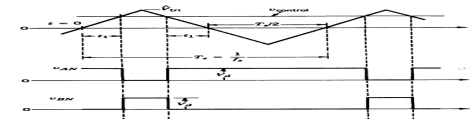


Figure 9: Bipolar Switching

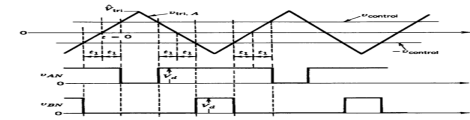


Figure 10: Unipolar switching

$m_a < 1$: linear, $m_a > 1$: overmodulation
||||| HEAD

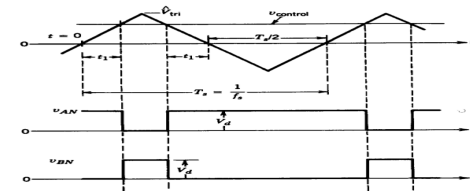


Figure 11: Bipolar Switching

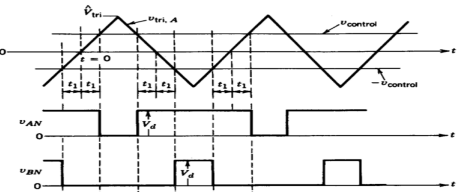


Figure 12: Unipolar switching

Cuk Converter

=====

llllllll

$$V_{c1} = V_o + V_d \tag{2}$$

Transformer Analysis

$$V_{rms} = \frac{2\pi}{\sqrt{2}} \cdot N_2 \cdot f \cdot B_{max} \cdot A \tag{3}$$